

Figure 4: Receiver mixer schematic diagram.

2. Mount and solder R93.
3. Mount and solder the capacitors, C90 and C91.
4. The power supply circuit of the oscillator is connected to VCC through a PTT (push-to-talk) switch and R93. A shunt capacitor (C93) to ground is added as a power supply bypass capacitor. Solder C93.
5. Mount and solder the push-button switch, S90.
6. We want this oscillator to operate only when we are transmitting. Therefore, we switch its power off during reception. But, for testing we will bypass the switch. A piece of wire was already soldered in the jumper position JP90. This jumper will be removed later, when testing is finished.
7. Solder a piece of wire in the GND jumper for a convenient ground connection.
8. Mount the transistor, Q90. Watch the orientation of the transistor. Solder it.
9. Apply the power to TRC-11. Measure the emitter voltage, V_E , at TP30. It should be close to 6 V. Turn off the power.

$$V_E = 5.33 \text{ V}$$

1.9. GRADE:

10. Mount and solder the 27.000 MHz quartz crystal, X90. We need a series capacitor, C94, to set the oscillation frequency at 27.000 MHz. Mount a 47 pF capacitor, but do not solder it yet. Make sure that capacitor leads touch the mounting holes. Without the capacitor connection the oscillator does not work.

11. Apply the power to TRC-11. Connect the oscilloscope probe to TP90. You should have an oscillation around 27.000 MHz. If the frequency is lower than ~~26.999~~ MHz, remove 47 pF and insert the next smaller standard capacitance. If it is higher than 27.001 MHz, insert the next larger standard capacitance. Solder the capacitor when the frequency is right. If the oscillation frequency is higher than 27.002 MHz ask for a different crystal from the lab technician.

30

Measure the frequency and the peak-to-peak voltage at TP30. Make sure that bandwidth limit of the oscilloscope is turned off. The peak-to-peak voltage should be larger than 1.5 V.

12. Replace the capacitor C35 (originally 10pF) with 180pF. This is needed to make sure that sufficiently high signal is fed to the RF amplifier.

C94=33₁F

Oscillation frequency=27.000MHz Peak-to-peak voltage=

4.52V

1.12. GRADE:

2. Amplitude Modulator

1. Most of the amplitude modulator is already built as given in Fig. 5. It uses a PNP transistor (Q31) to modulate the supply voltage of the transmitter amplifier (Q30). The only missing components are R34 (2.2K) and C32 (10 μ F). Mount and solder them. They connect the input of the modulation amplifier to the microphone amplifier output.

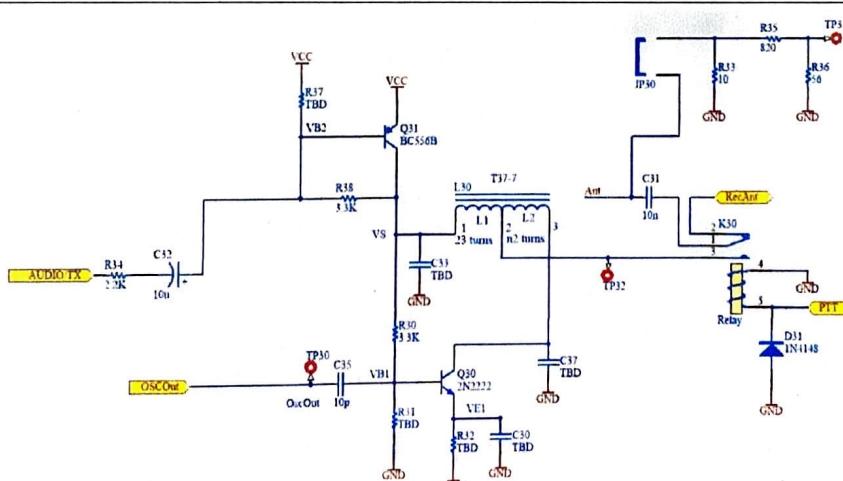


Figure 5: Schematic of the Amplitude modulator of TRC-11.

2. Cut the jumper wire of JP12 in the microphone amplifier section. This action will disconnect the microphone.
3. Connect the signal generator cable between TP11 and GND. Set its magnitude to 10 mV and its frequency to 1 KHz.

4. Apply the power. Observe the signal between TP12 and GND. You should see an undistorted sine wave.
5. Observe the signal between JP30 and GND. You should see an amplitude modulated (AM) 27.000 MHz signal. Set your oscilloscope time scale to 500 μ s/div. Set the ACQUIRE mode to Peak-detect. This setting allows the oscilloscope to capture the peak of the RF signal even though the sampling rate of the oscilloscope is not enough to capture the RF signal itself. Increase the signal amplitude until AM signal gets distorted. At this point, determine the modulation index, m , of the AM signal using the following equation

$$m = \frac{V_{max} - V_{min}}{2(V_{max} + V_{min})}$$

where V_{max} is the maximum peak-to-peak voltage, V_{min} is the minimum peak-to-peak voltage of the amplitude modulated signal.

$V_{max} = 1.06\text{V}$	$V_{min} = -1.0\text{V}$	$m = 17.16$
--------------------------	--------------------------	-------------

2.5. GRADE:

3. Receiver Mixer

1. Install and solder IC80, the receiver mixer. Make sure that pin 1 gets installed into the rectangular shaped pad on the PCB. Note that all other pads are oval shaped. This mixer converts 27.000 MHz signal to 15.000 MHz. The pin OSC_B of the mixer chip has a negative input resistance at high frequencies, if small capacitors (C82 and C83) are connected at pins OSC_B and OSC_E . When a quartz crystal resonator at 12.000 MHz is connected to this pin as shown in Fig. 4, an oscillator at 12.000 MHz is obtained.
2. Install and solder X80, C80, C81, C83, R80, and R81.
3. Mount and solder C82 such that it can be removed easily.
4. Solder looped pieces of wires to TP81 and TP85.
5. Solder C84 and C85.
6. Use 0.35 mm wire to wind 12 turns on T37-7 core to make L80. Install and solder L80.
7. Install and solder the jumper wire JP81.
8. Switch the power on. Measure and record the DC supply voltage at pin 8 (TP81). It should be slightly less than 6 V due to the voltage drop on R80. Measure the DC voltages at two input pins, 1 and 2. They should be equal and between 1.0 V to 1.7 V. Measure the DC voltages at the two output pins, 4 and 5. The voltages should be equal and between 2 V to 5.5 V. If you cannot measure these voltages, there is something wrong with your circuit.

IC80 pin 8 = 5.45V	pin 1 = 1.282V	pin 2 = 1.284V
--------------------	----------------	----------------

IC80 pin 4 = 2.975V	pin 5 = 2.974V
---------------------	----------------

3.8. GRADE:

9. Connect the oscilloscope probe (in $10\times$ setting) to TP85. You should be able to see an oscillation around 12.000 MHz. Measure the frequency of the oscillation with a 1 KHz accuracy. If the frequency is lower than 11.999 MHz, change the capacitor C82 to the next smaller standard value. If the frequency is higher than 12.001 MHz, change C82 to the next larger value. Record the capacitor value and the oscillation frequency
10. Measure the amplitude of the oscillation.

C82= 39 pF Frequency= 11.9995 MHz p-p amplitude= 1.60 V

3.10. GRADE:


11. Make sure that the jumper JP90 is cut.
12. Since your receiver is now ready, you can test it. Apply the power to TRC-11. Watch the red signal presence indicator LED. It should be off, indicating that there is no 27.000 MHz transmitter signal nearby.
We need a very very small signal to test the receiver. Set the signal generator to frequency to 27.000 MHz with an amplitude of $V_g=100\text{ mVpp}$. Connect the signal generator between TP31 and GND. Turn on the generator. The signal presence indictor LED should turn on. Note that if there are other transmitters nearby, your LED may be turned on even without applying the input voltage. If the signal presence indictor LED does not turn on even with 100 mVpp signal generator, you have something wrong in the receiver or it is not adjusted well.
13. Connect Ch-1 probe between TP70 and GND. This is the test point showing the AGC detector output. Change the frequency in 1 KHz steps to find the center frequency, f_{center} , of the receiver. When the voltage at TP70 is maximum, record that frequency.

$f_{center}=27.001\text{ 000 MHz}$

14. Record the DC voltage amplitude at TP70, V_{AGC} , as a function of signal amplitude, V_g , at this frequency. Note that you can use MEASURE button of the oscilloscope in Ch1 Mean position to read the AGC output voltage. Change the signal generator output from 10 mV_{pp} to 1810 mV_{pp} . Change the amplitude in 3-dB steps (14 mV , 20 mV , 28 mV , 40 mV , 57 mV , 80 mV , 113 mV , 160 mV , etc.) The AGC output voltage should be more and more positive as the signal generator output voltage is increased.

Plot V_{AGC} as a function of V_g on a semilog paper.

V_g (mV _{pp})	V_{AGC} (V)	V_g (mV _{pp})	V_{AGC} (V)
10	370 mV	160	2.6 V
14	400 mV	226	2.7 V
20	480 mV	320	3.2 V
28 (00 mV)	453		3.5 V
40	950 mV	640	3.6 V
57	1.6 V	905	3.6 V
80	2.5 V	1280	3.6 V
113	2.54 V	1810	3.6 V

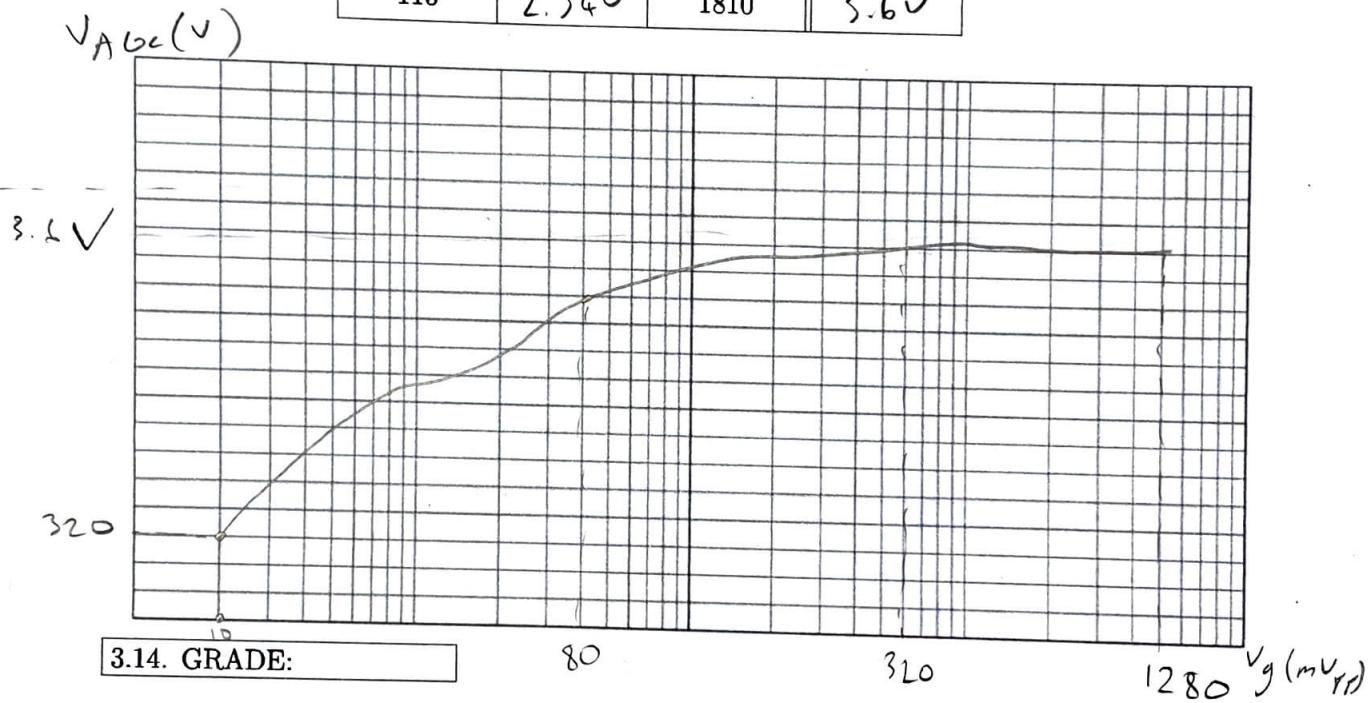

15. Recall that the mixer adds or subtracts the two frequencies. Since the local oscillator frequency is 12 MHz, an image frequency of 3 MHz will create a sum frequency of $3+12=15$ MHz, which will go through the quartz crystal IF filter. However, the receiver's input RF tuner is tuned to 27 MHz, and it hopefully rejects 3 MHz and reduce the gain at that frequency.

Let us find the image rejection ratio of your receiver at the image frequency of 3 MHz. Set the signal generator to 3 MHz and amplitude at 2 V_{pp}. Connect the signal generator cable between TP31 and GND. Connect the oscilloscope probe to TP70, the AGC output voltage. Change the frequency in 1 KHz steps to maximize the AGC output voltage. Record that frequency as f_{image} . If the AGC output voltage is zero, increase the signal generator voltage until you see a voltage. Adjust the amplitude such that you have the same AGC output voltage as the 0.02=20 mV_{pp} signal at 27 MHz (which is recorded in the previous step). Record that amplitude, $V_{g,image}$. Find the image rejection ratio of your receiver in dB using

$$IR_{dB} = 20 \log_{10} \frac{V_{g,image}}{0.02}$$

$$f_{image} = 3.000 \text{ MHz}$$

$$IR_{dB} = 44.1 dB$$

3.15. GRADE:

If you have trouble with your receiver, refer to Appendix J at page 440 for TRC-11 troubleshooting.

16. If your transmitter and receiver is QK cut the jumper wire at JP30. TRC-11 is ready to go on the air!

CHECK POINT: