

$$V_- = \frac{R_1}{R_1 + R_2} \cdot V_{out}$$

$$\frac{A \cdot (V_{in} - \beta \cdot V_{out})}{R_{out}} = \frac{V_{out} - \beta \cdot V_{out}}{R_2}$$

$$\frac{A \cdot V_{in}}{R_{out}} = \frac{A \cdot \beta \cdot V_{out}}{R_{out}} + \frac{V_{out}}{R_2} - \frac{\beta \cdot V_{out}}{R_2}$$

$$\frac{A \cdot V_{in}}{R_{out}} = V_{out} \left(\frac{A \cdot \beta}{R_{out}} + \frac{1}{R_2} - \frac{\beta}{R_2} \right)$$

$$A \cdot V_{in} = V_{out} \left(A \beta + \frac{(1 - \beta) R_{out}}{R_2} \right)$$


$$= \frac{4 \cdot 1000}{4 \cdot 1000 \cdot \frac{1}{5} + (0.8) 100} = 4.54$$

(a)
$$\frac{V_{out}}{V_{in}} = \frac{A \cdot R_2}{A \cdot \beta \cdot R_2 + (1 - \beta) R_{out}}$$

(b) $R_{out} = 0$, A is very large, $\frac{V_{out}}{V_{in}} \approx \frac{1}{\beta} = 5$

(c) As it can be seen from the equation in part (a) R_{out} has a significant role in determining the closed loop gain hence with comparable R_{out} to R_L the loading does not occur and OPAMP operates as desired.

Question 2

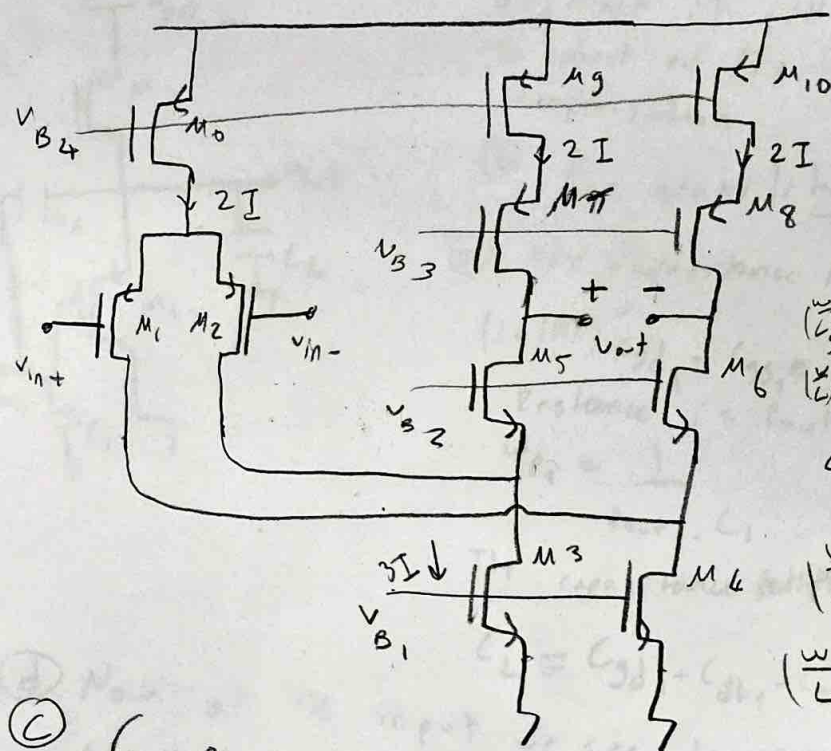

$$\mu_n C_{ox} = 4 \mu_p C_{ox}, \gamma = 0$$

$$r_{o5} = r_{o1} \quad g_{m5} = g_{m1} \quad \lambda_n = \lambda_p$$

$$(w/L)_5 = (w/L)_6$$

(a) CS inverts Common gate does not

$$(b) \left(\frac{w}{L}\right)_0 = \left(\frac{w}{L}\right)_9 = \left(\frac{w}{L}\right)_{10}$$

$$\left(\frac{w}{L}\right)_1 \frac{1}{2} \mu_p C_{ox} (V_{ov})^2 = 2I = \left(\frac{w}{L}\right)_8 = \left(\frac{w}{L}\right)_7$$

$$\left(\frac{w}{L}\right)_5 \frac{1}{2} \mu_n C_{ox} (V_{ov})^2 = 2I$$

$$4 \cdot \left(\frac{w}{L}\right)_5 = \left(\frac{w}{L}\right)_9$$

$$\left(\frac{w}{L}\right)_5 = \left(\frac{w}{L}\right)_6 = \frac{2}{3} \left(\frac{w}{L}\right)_3 = \frac{2}{3} \left(\frac{w}{L}\right)_4$$

$$\left(\frac{w}{L}\right)_1 = \left(\frac{w}{L}\right)_2 = 2 \cdot \left(\frac{w}{L}\right)_0$$

(c) $G_m \approx g_{m2}$, $R_{out} = \underbrace{g_{m7} r_{o7} r_{o7}}_{\text{Simplification of } r_{s1} + r_{o1}(1+g_{m2}r_{o1})} \parallel g_{m5} r_{o5} (r_{o3} \parallel r_{o4})$

$$A_v = \left| \frac{v_{out}}{v_{in}} \right| = g_{m2} \cdot R_{out}$$

$$A_v = g_{m1} \cdot (g_{m1} r_{o1}^2 \parallel g_{m1} \frac{r_{o1}^2}{2})$$

$$A_v = g_{m1} \cdot \frac{2 g_{m1} r_{o1}^2}{3} = 2 \frac{g_{m1}^2 r_{o1}^2}{3}$$

$$g_{m5} = \sqrt{2I_{D1} \cdot \left(\frac{w}{L}\right)_5 \cdot \mu_p C_{ox}}$$

$$g_{m7} = \sqrt{2I_{D1} \cdot \left(\frac{w}{L}\right)_7 \cdot \mu_p C_{ox}}$$

$$g_{m7} = g_{m5} = g_{m1}$$

$$g_{m2} = \sqrt{I_{D1} \cdot \left(\frac{w}{L}\right)_2 \cdot \mu_p C_{ox}}$$

$$g_{m2} = g_{m7} = g_{m1}$$

(d) Short v_{in-} and v_{out} , (1) $V_{B3} > V_{out} - V_{th}$

$$V_{B3} + V_{th} > V_{in} > V_{B2} - V_{ov} - 2V_{th}$$

(2) $V_{out} > V_{B2} - V_{th}$, $V_{B2} - V_{ov} + V_{th} < V_{in}$


(3) $\underbrace{\hspace{2cm}}$ greater than (2)

(e) From M_2 , $\frac{4k\epsilon\epsilon_0}{g_{m2}}$, From M_3 , $\frac{4k\epsilon\epsilon_0 g_{m3} (R_{out})^2}{g_{m2}^2 \cdot (R_{out})^2}$

From M_9 , $\frac{4k\epsilon\epsilon_0 g_{m9} (R_{out})^2}{g_{m2}^2 \cdot (R_{out})^2}$, $V_{nin} = \left(\frac{4k\epsilon\epsilon_0}{g_{m2}} + \frac{4k\epsilon\epsilon_0 g_{m3}}{g_{m2}^2} + \frac{4k\epsilon\epsilon_0 g_{m9}}{g_{m2}^2} \right) 2$

Middle transistors do not contribute to noise due to source degeneration noise is not amplified.

Question 3

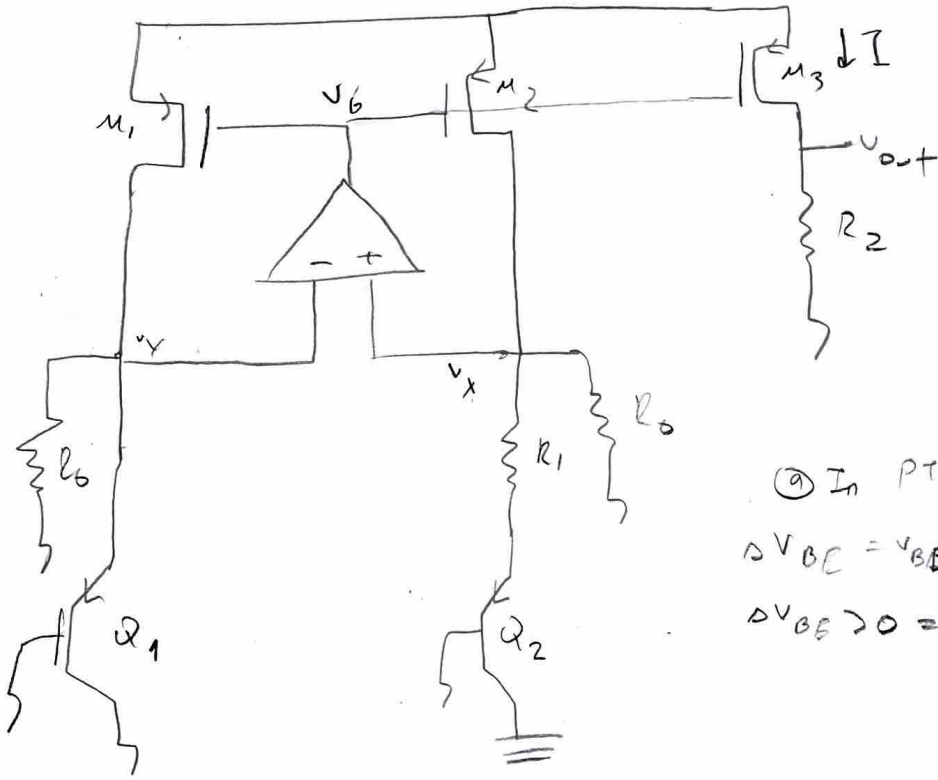

(a) In PTAT behaviour $\Delta V_{BE} > 0$

$$\Delta V_{BE} = V_{BE1} - V_{BE2} = V_T \ln(n) \rightarrow A_2$$

$$\Delta V_{BE} > 0 \Rightarrow n \cdot A_1 = A_2 \quad \overline{A_1}$$

(b) we need to verify that when $V_x \uparrow$, $V_{out} \downarrow$.


when $V_x \uparrow$, $A \cdot (V_x - V_y) = V_G \uparrow$, As $V_G \uparrow$ $V_{SG} \downarrow$ hence $I \downarrow$

$V_{out} = I_2 \cdot R_2$, $V_{out} \downarrow$. Therefore negative feedback is available

(c) $V_x = V_y$, $I \cdot R_1 + V_{EB2} = V_{EB1}$, $I \cdot R_1 = V_T \cdot \ln(n)$, $I \cdot R_2 = V_{0.1}$

$$V_{out} = \frac{R_2}{R_1} \cdot V_7 \ln(n)$$

Question 4

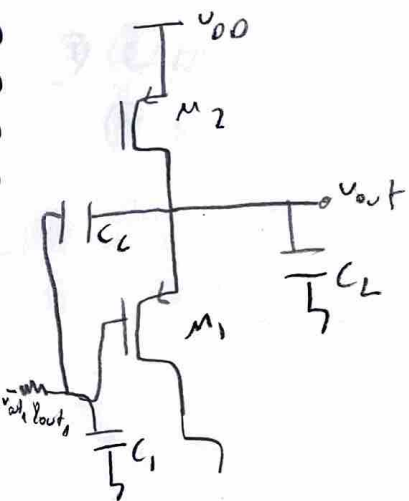

(a) 2 poles does not ~~cross~~ exceed -180° degrees
at most it will reach -180° and oscillate
So most of the cases it does not require compensation

(b) For stability

(c) The capacitance from M_1

$(1+|A|)C_{gd1} + C_{gs1}$, Total cap at the gate of M_1
Resistance is R_{out1}

$$\omega_{p1} = \frac{1}{R_{out1} \cdot C_1}$$

$$C_1 = (1+|A|)C_{gd1} + C_{gs1}$$

The capacitance at the output is

$$C_L = C_{gd1} + C_{db1} + C_{gs2} + C_{sb2} = C_L, \quad \omega_{p2} = \frac{1}{(r_{o2} || r_{o1}) \cdot C_L}$$

(d) Now at the input we see $(1+|A|)C_L + C_1$ as the cap.
At the output we see $C_L + C_C$ as the cap

$$\omega_{p1, new} = \frac{1}{R_{out1} (C_1 + (1+|A|)C_L)}$$

moves to lower freq


$$\omega_{p2, new} \approx \frac{g_m}{C_C}$$

moves to higher freq

Question 5

(a) (i) $A \rightarrow R_A = \frac{1}{g_m} \parallel r_o = \frac{1}{g_m}$ $\omega_{pA} = \frac{g_m}{C_A}$ $C_A = C_{gs3} + C_{gd3} + C_{db1} + C_{gd1} + C_{gs4} + C_{gd4}(1-A) - g_m \frac{r_o}{2}$
 (ii) out $\rightarrow R_{out} = r_o \parallel r_o = \frac{r_o}{2}$ $\omega_{pout} = \frac{2}{r_o \cdot C_{out}}$ $C_{out} = C_{db4} + C_{gd4} + C_{db2} + C_{gd2}$

(b)

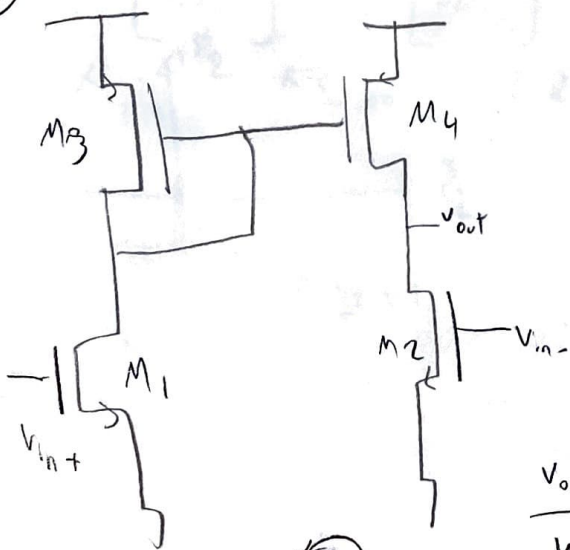

$v_{in+} \rightarrow v_{out}$ gain is $\uparrow g_m \frac{1}{1m}$
 $\textcircled{1} \cdot g_m \frac{r_o}{2}$

$v_{in-} \rightarrow v_{out}$ gain is $-g_m \frac{r_o}{2}$

$$\frac{v_{out}(s)}{v_{in+}} = \frac{g_m r_o}{2} \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pA}}} \right) \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pO}}} \right)$$

$$\frac{v_{out}(s)}{v_{in-}} = -\frac{g_m r_o}{2} \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pO}}} \right)$$

$$\frac{v_{out}(s)}{v_{in}} = \frac{g_m r_o}{2} \cdot \left(\frac{1}{1 + \frac{s}{\omega_{pout}}} \right) \cdot \left(1 + \frac{1}{1 + \frac{s}{\omega_{pA}}} \right)$$

$$\frac{v_{out}(s)}{v_{in}} = \frac{g_m r_o}{2} \cdot \frac{(2 + \frac{s}{\omega_{pA}})}{(1 + \frac{s}{\omega_{pout}})(1 + \frac{s}{\omega_{pA}})}$$

zero at $2\omega_{pA}$
 $= 2 \frac{g_m}{C_A}$