

**EEE102 LAB06:Greatest Common Divisor****Purpose:**

Aim of this experiment is to design a 8 bit greatest common divisor finder by using subtractors, comparators and registers.

**Research Questions:**

-What was your algorithm to calculate the GCD?

Simplified Euclidean Algorithm is used to calculate GCD.

-Is your module a combinational circuit or an FSM? If the latter, is it a Moore machine or a Mealy machine? Would it be cheaper to implement GCD as a combinational circuit or as an FSM? Would it be faster? What are the drawbacks in each case?

My module is FSM, Moore Machine. Even though combinational circuits are faster and cheaper than FSM. In this design memory elements are included. Keeping the memory or registering new values are much simpler with FSM however it can not be said that FSM is cheaper and faster than combinational circuit.


-How many clock cycles did it take in your simulation to calculate the GCD? Do you think this can be optimized? How so?

It took 296 clock cycles. By reducing operations with clock input, amount of clock cycles can be optimized.

**Methodology:**


Greatest common divisor algorithm is designed by using a subtractor and comparator. Initially, the design compares two 8 bit numbers by the 3 bit output (010-equal, 001-greater, 100 lesser). And if they are not equal smaller one is subtracted from the greater one until both numbers are equal (Simplified Euclidean Algorithm). When they are equal the output is demonstrated on assigned LEDs as the output which is greatest common divisor. The process is initialized by U17 button which is assigned to "start". To find the greatest common divisor of another pair reset button is assigned to T18. Comparator is designed by obtaining every bit for the output in terms of inputs' bits by Karnaugh Map. Then, with using logic gates output for the comparator is obtained. Subtractor was obtained from LAB04. In gcd file, obtained values from subtraction are registered as new input until both of the inputs are equal. Testbench is written in order to obtain simulation for a better understanding and design is implemented to BASYS3.

## RTL Schematic:

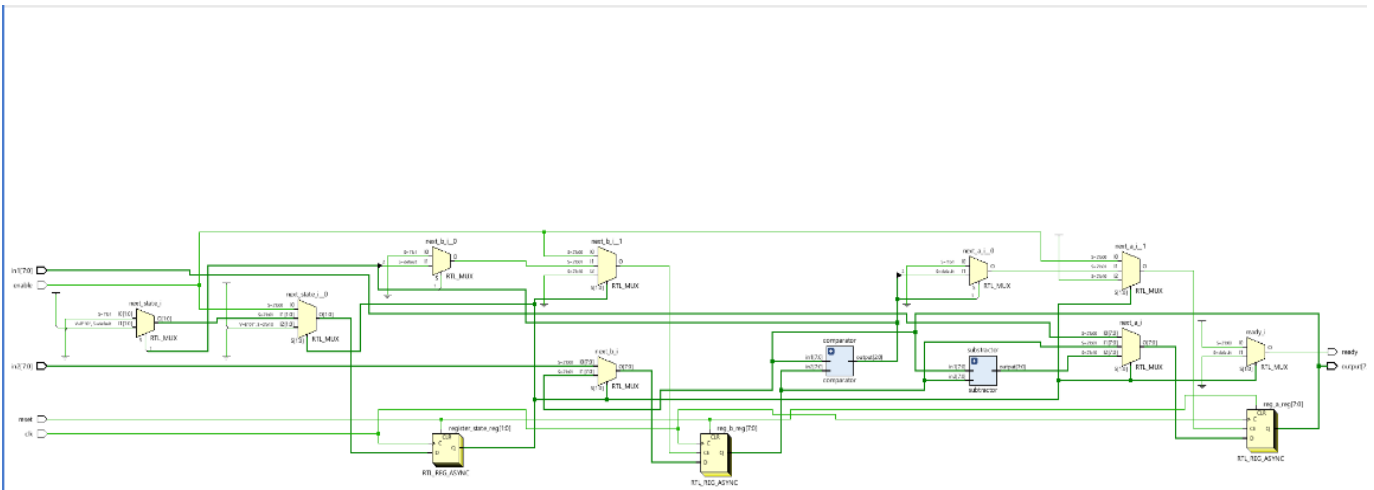


RTL schematic of greatest common divider finder(gcd)

## Simulation:

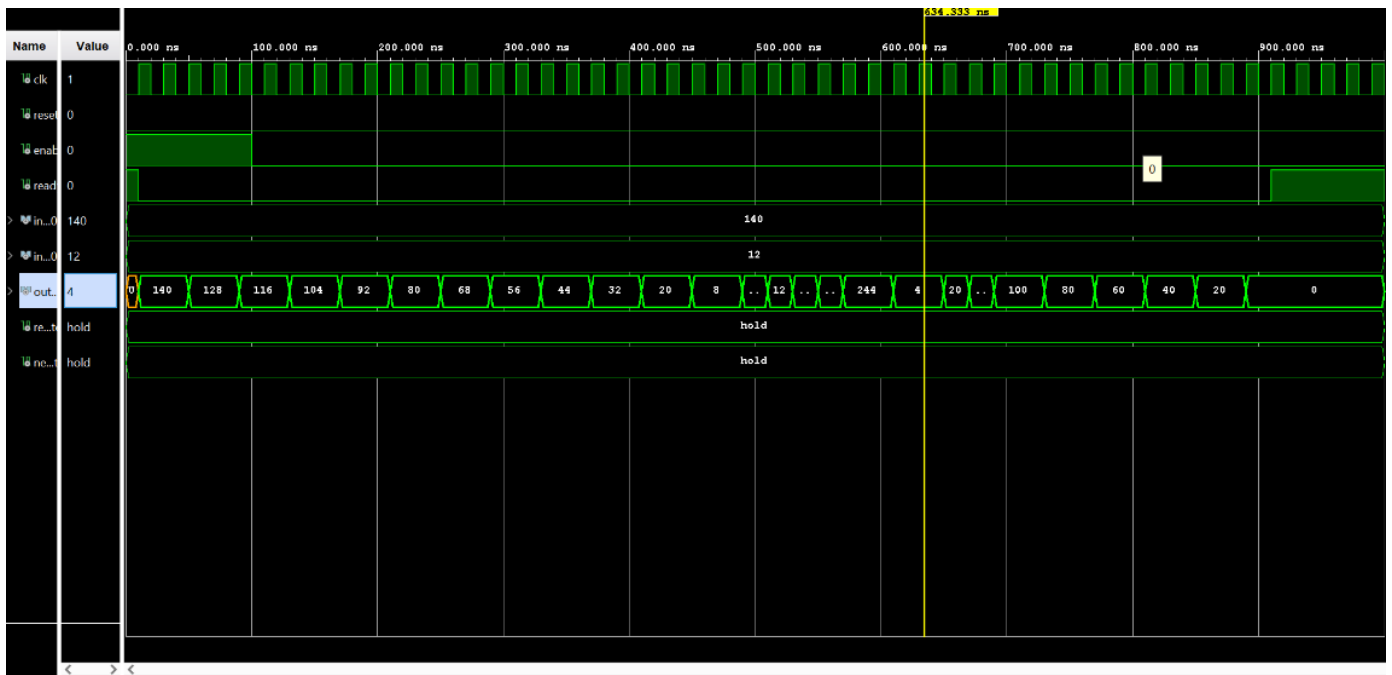


Simulation of in1="10001100" and in2="00001100"


## BASYS3 Demonstration:

 

 in1="00000010",in2="00000100",output="00000010",ready="1"



 in1="1001100",in2="00001100",output="00000100",ready="1"



in1="00110000",in2="00000100",output="00000100",ready="1"

### Conclusion:

In this experiment, greatest common divisor is found by using Simplified Euclidean Algorithm. Subtractor and comparator was necessary to use this algorithm. Demonstration on BASYS3 was successful and I feel more confident using registers in my designs.

## Appendix:

### Code of subtractor

```
library ieee;

use ieee.std_logic_1164.all;

entity subtractor is
    port (in1, in2: IN STD_LOGIC_VECTOR ( 7 DOWNT0 0);
    output : OUT STD_LOGIC_VECTOR ( 7 DOWNT0 0);

    tst: out std_logic
);
end subtractor;

architecture behavioral of subtractor is
    signal b1,b2,b3,b4,b5,b6,b7,b8: std_logic;
BEGIN

    tst <= in1(0) XOR in2(0) xor '0';
    output(0) <= in1(0) XOR in2(0) xor '0';
    b1 <= (not(in1(0)) and '0') or (not(in1(0)) and in2(0)) or (in2(0) and '0');
    output(1) <= in1(1) XOR in2(1) xor b1;
    b2 <= (not(in1(1)) and b1) or (not(in1(1)) and in2(1)) or (in2(1) and b1) ;
    output(2) <= in1(2) XOR in2(2) xor b2;
    b3 <= (not(in1(2)) and b2) or (not(in1(2)) and in2(2)) or (in2(2) and b2);
    output(3) <= in1(3) XOR in2(3) xor b3;
    b4 <= (not(in1(3)) and b3) or (not(in1(3)) and in2(3)) or (in2(3) and b3);
    output(4) <= in1(4) XOR in2(4) xor b4;
    b5 <= (not(in1(4)) and b4) or (not(in1(4)) and in2(4)) or (in2(4) and b4);
    output(5) <= in1(5) XOR in2(5) xor b5;
    b6 <= (not(in1(5)) and b5) or (not(in1(5)) and in1(5)) or (in2(5) and b5);
    output(6) <= in1(6) XOR in2(6) xor b6;
    b7 <= (not(in1(6)) and b6) or (not(in1(6)) and in2(6)) or (in2(6) and b6);
    output(7) <= in1(7) XOR in2(7) xor b7;

END behavioral;
```

**Code of comparator:**

```
library ieee;

use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity comparator is
    port (
        in1, in2: in unsigned(7 downto 0);
        output: out std_logic_vector(2 downto 0)
    );
end entity;

architecture behavioral of comparator is
    signal equal1: std_logic_vector(7 downto 0);
    signal great1, great2: std_logic;
    signal result: std_logic_vector(2 downto 0);
    signal equal2, grtr, lssr: std_logic;
begin

    equal1(0) <= (not in1(0)) xnor (not in2(0));
    equal1(1) <= (not in1(1)) xnor (not in2(1));
    equal1(2) <= (not in1(2)) xnor (not in2(2));
    equal1(3) <= (not in1(3)) xnor (not in2(3));
    equal1(4) <= (not in1(4)) xnor (not in2(4));
    equal1(5) <= (not in1(5)) xnor (not in2(5));
    equal1(6) <= (not in1(6)) xnor (not in2(6));
    equal1(7) <= (not in1(7)) xnor (not in2(7));

    equal1ual2<= '1' when equal1 = x"FF" else '0';

    grtr <= (in1(7) and not(in2(7)))or
    (in1(6) and not(in2(6)) and equal1(7))or
    (in1(5) and not(in2(5)) and equal1(7) and equal1(6))or
```

```

(in1(4) and not(in2(4)) and equal1(7) and equal1(6) and equal1(5))or
(in1(3) and not(in2(3)) and equal1(7) and equal1(6) and equal1(5) and equal1(4))or
(in1(2) and not(in2(2)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3))or
(in1(1) and not(in2(1)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3) and
equal1(2))or
(in1(0) and not(in2(0)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3) and
equal1(2) and equal1(1));
lssr <= (in2(7) and not(in1(7)))or
(in2(6) and not(in1(6)) and equal1(7))or
(in2(5) and not(in1(5)) and equal1(7) and equal1(6))or
(in2(4) and not(in1(4)) and equal1(7) and equal1(6) and equal1(5))or
(in2(3) and not(in1(3)) and equal1(7) and equal1(6) and equal1(5) and equal1(4))or
(in2(2) and not(in1(2)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3))or
(in2(1) and not(in1(1)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3) and
equal1(2))or
(in2(0) and not(in1(0)) and equal1(7) and equal1(6) and equal1(5) and equal1(4) and equal1(3) and
equal1(2) and equal1(1));
result(2) <= lssr;
result(0) <= grtr;
result(1) <= equal2;
output <= result;
end behavioral;

```

## Code of gcd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity gcd is
port(
    clk, reset: in std_logic;
    enable: in std_logic;
    in1, in2: in std_logic_vector(7 downto 0);
    ready: out std_logic;
    output: out std_logic_vector(7 downto 0)
);
end gcd ;

architecture behavioral of gcd is
    type state_type is (hold, replace, subtract);
    signal register_state, next_state : state_type;

    signal reg1, reg2, next1, next2: unsigned(7 downto 0);
    signal comp1, comp2 : unsigned(7 downto 0);

    signal subs_2, subs_1, subs_out: std_logic_vector(7 downto 0);
    signal comp_out: std_logic_vector(2 downto 0);

begin
    -----

    comparator: entity work.comparator(behavioral)
    port map(in1 => comp1, in2=> comp2, output=> comp_out);

    subtractor: entity work.subtractor(behavioral)
```



```
port map(in1 => subs_1, in2 => subs_2, output => subs_out);
```

```
-----  
process(clk,reset)
```

```
begin
```

```
if reset='1' then
```

```
    register_state <= hold;
```

```
    reg1 <= (others=>'0');
```

```
    reg2 <= (others=>'0');
```

```
elseif (rising_edge(clk)) then
```

```
    register_state <= next_state;
```

```
    reg1 <= next1;
```

```
    reg2 <= next2;
```

```
end if;
```

```
end process;
```

```
-----  
process(register_state,reg1,reg2,enable,in1,in2)
```

```
begin
```

```
    next1 <= reg1;
```

```
    next2 <= reg2;
```

```
    comp1 <= reg1;
```

```
    comp2 <= reg2;
```

```
    subs_1 <= std_logic_vector(reg1);
```

```
    subs_2 <= std_logic_vector(reg2);
```

```
case register_state is
```

```
-----  
when hold =>
```

```
    if enable = '1' then
```

```
        next1 <= unsigned(in1);
```

```
        next2 <= unsigned(in2);
```

```
        next_state <= replace;
```

else

next\_state <= hold;

end if;

-----  
when replace =>

if (comp\_out(1) = '1') then

next\_state <= hold;

else

if(comp\_out(2) = '1') then

next1 <= reg2;

next2 <= reg1;

end if;

next\_state <= subtract;

end if;

-----  
when subtract =>

next1 <= unsigned(subs\_out);

next\_state <= replace;

end case;

end process;

-----  
ready <= '1' when register\_state = hold else '0';

output <= std\_logic\_vector(reg1);

-----  
end behavioral;

### Code of testbench

```
library ieee;

use ieee.std_logic_1164.all;

-----

entity testbench1 is
end testbench1;

-----

architecture behavioral of testbench1 is

    signal clk, reset, enable, ready: std_logic;
    signal in1, in2, output : std_logic_vector (7 downto 0);
    type state_type is (hold, replace, subtract);
    signal register_state, next_state : state_type;

begin
    -----

    dut: entity work.gcd(behavioral)
    port map(clk, reset, enable, in1, in2, ready, output);
    -----

    clock_process: process begin
        clk <= '0';
        wait for 10ns;
        clk <= '1';
        wait for 10ns;
        end process;
    -----

    stim_process: process begin
        enable <= '1';
        in1 <= "10001100";
        in2 <= "00001100";
        reset <= '0';
        wait for 100ns;
        enable <= '0';
```

wait;

end process;

-----  
end behavioral;

-----  
configuration behavioral of testbench1 is

for behavioral

end for;

end behavioral;

### **Code of constraints**

set\_property PACKAGE\_PIN W5 [get\_ports clk]

set\_property IOSTANDARD LVCMOS33 [get\_ports clk]

create\_clock -add -name sys\_clk\_pin -period 10.00 -waveform {0 5} [get\_ports clk]

# Switches

set\_property PACKAGE\_PIN V17 [get\_ports {in1[0]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[0]}]

set\_property PACKAGE\_PIN V16 [get\_ports {in1[1]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[1]}]

set\_property PACKAGE\_PIN W16 [get\_ports {in1[2]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[2]}]

set\_property PACKAGE\_PIN W17 [get\_ports {in1[3]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[3]}]

set\_property PACKAGE\_PIN W15 [get\_ports {in1[4]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[4]}]

set\_property PACKAGE\_PIN V15 [get\_ports {in1[5]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[5]}]

set\_property PACKAGE\_PIN W14 [get\_ports {in1[6]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[6]}]

set\_property PACKAGE\_PIN W13 [get\_ports {in1[7]}]

set\_property IOSTANDARD LVCMOS33 [get\_ports {in1[7]}]

```
set_property PACKAGE_PIN V2 [get_ports {in2[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[0]}]
set_property PACKAGE_PIN T3 [get_ports {in2[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[1]}]
set_property PACKAGE_PIN T2 [get_ports {in2[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[2]}]
set_property PACKAGE_PIN R3 [get_ports {in2[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[3]}]
set_property PACKAGE_PIN W2 [get_ports {in2[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[4]}]
set_property PACKAGE_PIN U1 [get_ports {in2[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[5]}]
set_property PACKAGE_PIN T1 [get_ports {in2[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[6]}]
set_property PACKAGE_PIN R2 [get_ports {in2[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[7]}]
```

# LEDs

```
set_property PACKAGE_PIN U16 [get_ports {output[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[0]}]
set_property PACKAGE_PIN E19 [get_ports {output[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[1]}]
set_property PACKAGE_PIN U19 [get_ports {output[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[2]}]
set_property PACKAGE_PIN V19 [get_ports {output[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[3]}]
set_property PACKAGE_PIN W18 [get_ports {output[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[4]}]
set_property PACKAGE_PIN U15 [get_ports {output[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[5]}]
set_property PACKAGE_PIN U14 [get_ports {output[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[6]}]
```

```
set_property PACKAGE_PIN V14 [get_ports {output[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {output[7]}]
set_property PACKAGE_PIN L1 [get_ports {ready}]
set_property IOSTANDARD LVCMOS33 [get_ports {ready}]
#Buttons
set_property PACKAGE_PIN T18 [get_ports reset]
set_property IOSTANDARD LVCMOS33 [get_ports reset]
set_property PACKAGE_PIN U17 [get_ports enable]
set_property IOSTANDARD LVCMOS33 [get_ports enable]
```