
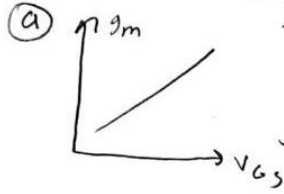


## EEE415 Spring 2024/25 Homework 1

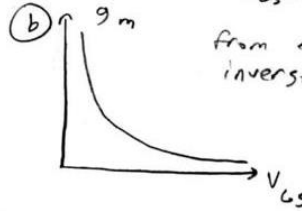
Q1)  $g_m = M_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{th}) = \sqrt{2 M_n C_{ox} \left( \frac{W}{L} \right) I_D} = \frac{2 I_D}{V_{GS} - V_{th}}$




from eq. (1)  
linear relation




from eq. (3)  
inversely parabolic

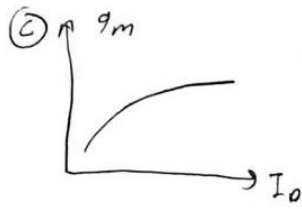


from eq. (2)  
"sqrt" relation

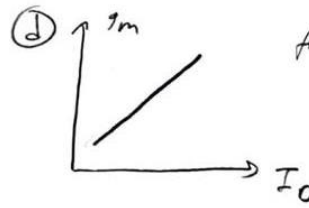

from eq. (3)  
linear.

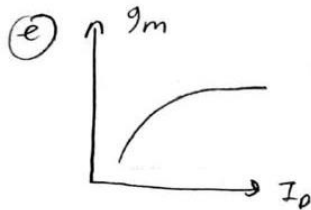


from eq. (2)  
"sqrt" relation

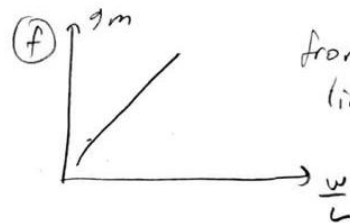


from eq. (1)  
linear.


Q2) a)

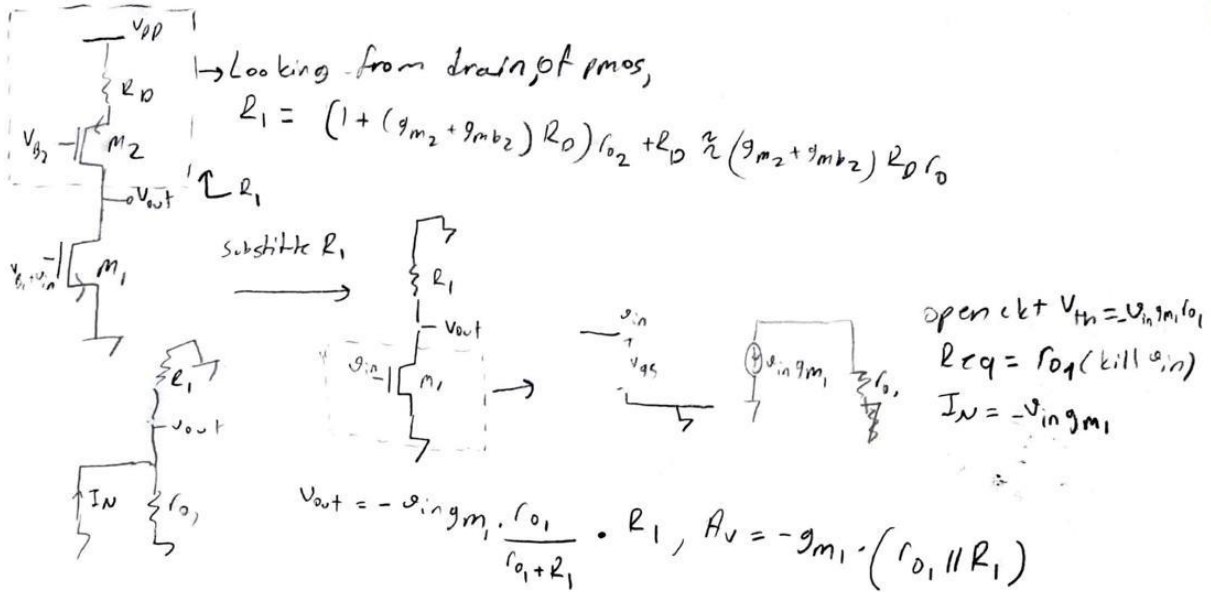

b)

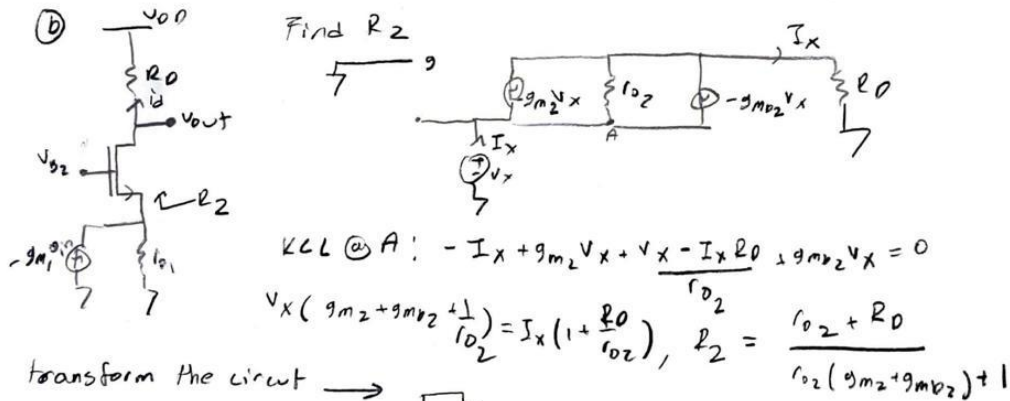


transform the circuit  $\rightarrow$

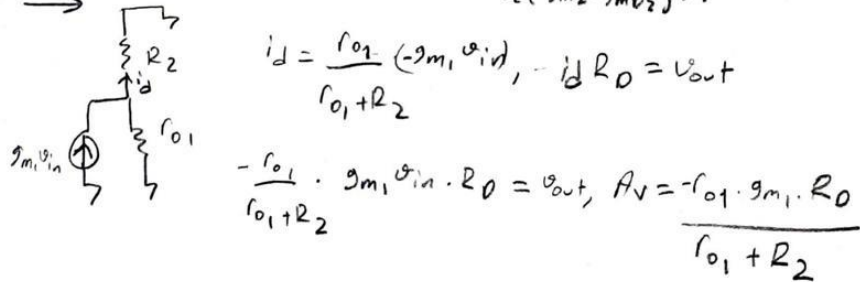

Q3) a) check  $V_{DS} > V_{GS} - V_{th}$  and  $V_{SD} > V_{SG} - |V_{th}|$

$0 > -V_{th} \rightarrow m_2$  is SAT  $V_{in} > -V_{th} \rightarrow m_1$  is SAT

For on-off conditions,  $m_1 \rightarrow V_{out} - V_{in} > |V_{th}| = V_{th}$ ,  $m_2 \rightarrow V_{DD} - V_{out} > V_{th}$

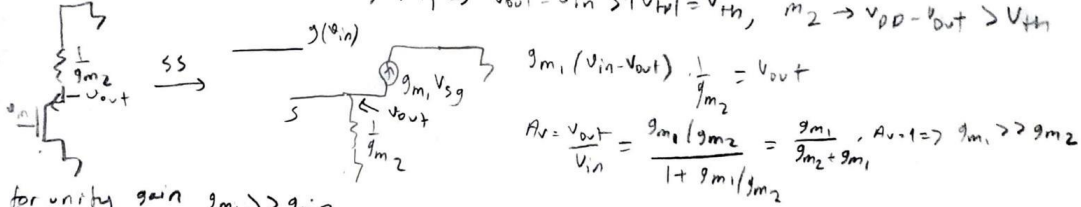


for unity gain  $g_{m1} \gg g_{m2}$


( $\beta=0, \lambda=0$ ) choose  $(\frac{W}{L})_1 > (\frac{W}{L})_2$

$$I_{D1} = \frac{\gamma}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{out} - V_{in} - V_{th})^2$$
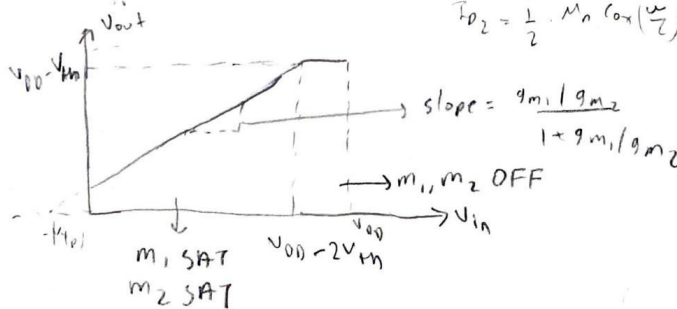
$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{th})^2$$



b) Design a source follower with 2 nmos.

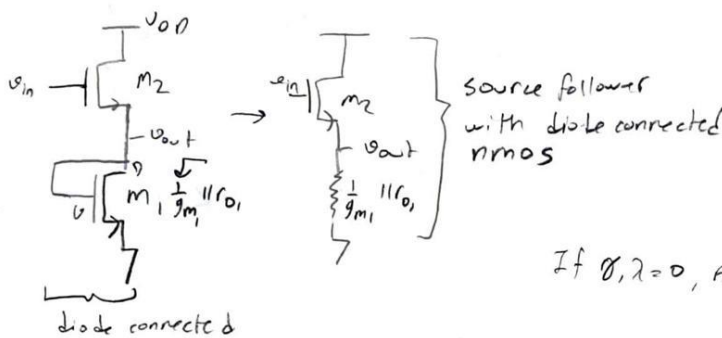

from Thevenin ckt.

$$A_v = \frac{R_{eq}}{\frac{1}{g_{m2}} + R_{eq}}$$

$$R_{eq} = r_{o1} || r_{o2} || \frac{1}{g_{mb2}} || \frac{1}{g_{m1}}$$

If  $\beta, \lambda=0$ ,  $A_v = \frac{g_{m2}}{g_{m2} + g_{m1}} \rightarrow$  same with part a) only transistor numbers are different.


- In pmos source follower  $m_1$  and  $m_2$  suffer from body effect whereas in 2 nmos source follower only  $m_2$  suffers from body effect.

c)  $m_2$  is in triode replace it with a resistor.





$$A_v = \frac{R_{eq}}{\frac{1}{g_{m1}} + R_{eq}} \rightarrow \text{if } \beta, \lambda=0 \text{ } A_v = \frac{g_{m1}}{g_{m2} + g_{m1}} \text{ holds with previous parts.}$$

Q4)

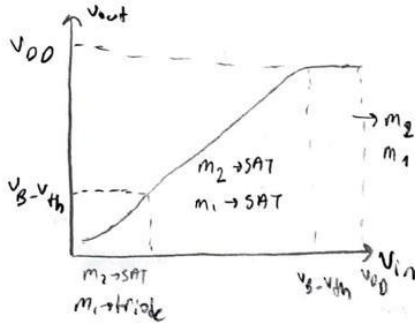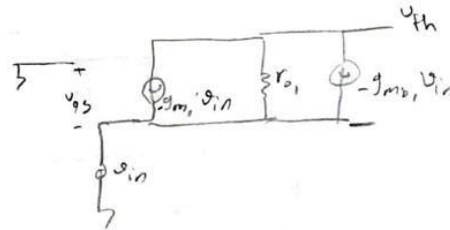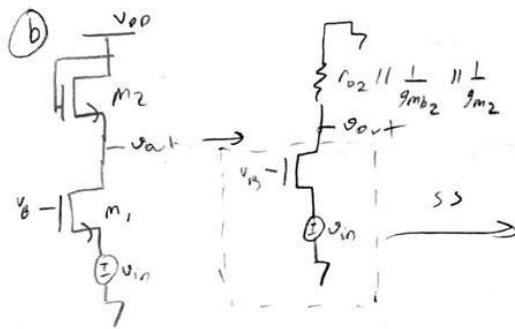 a)  $m_2$  always in SAT.  $\rightarrow 0 > -v_{th}$ ,  $v_{in} \uparrow \rightarrow v_{gs1} \downarrow \rightarrow I_{D1} \downarrow \Rightarrow I_{D2} \downarrow \Rightarrow v_{out} \uparrow$ , positive gain.


$v_o - v_{in} > v_{B} - v_{in} - v_{th}$ ,  $v_{DD} - v_o > v_{th}$   
 Around small  $v_{in}$ ,  $m_1$  produces large current +  
 hence  $v_{GS2}$  should be large hence,  $v_{out}$  is small  
 $v_o > v_{B} - v_{th} \Rightarrow m_1$  goes from triode to SAT  
 check  $v_{GS1} > v_{th} \rightarrow v_{B} - v_{in} > v_{th}$ ,  $v_{B} - v_{th} > v_{in}$   
 for  $m_1$   
 for  $v_{in} > v_{B} - v_{th}$   $m_1$  turns off. Also since  
 $v_{GS2} = 0 < v_{th}$  ( $v_{out} = v_{DD}$ ),  $m_2$  turns off




$$I_X = \frac{v_X}{r_{o1}}, R_{th} = r_{o1}$$



$$-g_{m1} v_{in} - g_{m2} v_{in} + \frac{v_{th} - v_{in}}{r_{o1}} = 0$$

$$\frac{v_{in}}{r_{o1}} = v_{in} (g_{m1} + g_{m2} + \frac{1}{r_{o1}}), v_{in} = v_{in} (r_{o1} (g_{m1} + g_{m2}) + 1)$$

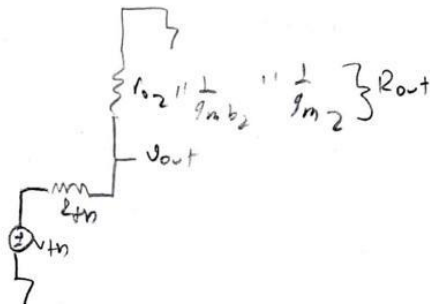
$$v_{out} = v_{th} \cdot \frac{R_{out}}{R_{th} + R_{out}}, A_v = (r_{o1} (g_{m1} + g_{m2}) + 1) \cdot \frac{R_{out}}{R_{th} + R_{out}}$$



Q5)

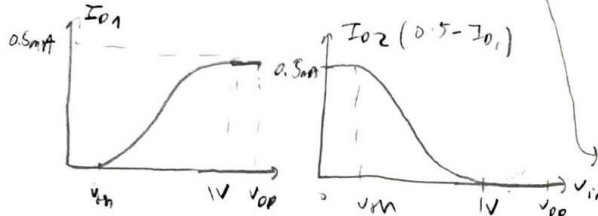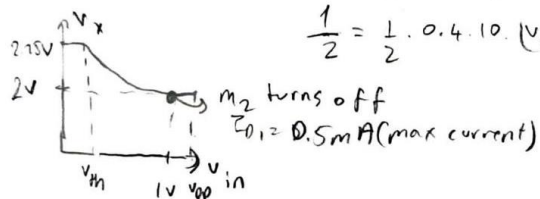 a)  $V_{in} = 0 \Rightarrow m_1$  is off,  $I_{D1} = 0$ ,  $I_{D2} = 0.5 \text{ mA}$ ,  $V_{out} = R_{D2} \cdot I_{D2} = 1.5 \text{ V}$ 
 $I_{D2} = \frac{1}{2} \cdot \mu_p C_{ox} \left( \frac{W}{L} \right)_2 \cdot (V_X - 1.5 - 0.5)^2$  Also  $V_{in} \uparrow \Rightarrow I_{D1} \uparrow \Rightarrow I_{D2} \downarrow \Rightarrow V_X \downarrow \Rightarrow V_{out} \downarrow$  negative gain

 when  $m_2$  turns off  
 $V_X - 1.5 < 0.5 \Rightarrow V_X < 2 \text{ V}$ 
 $I_{D2} = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_X - 2)^2$ ,  $V_X = 2 \Rightarrow I_{D2} = 0$   
 $V_X = 2.25 \text{ V}$  (max  $V_X$  value)

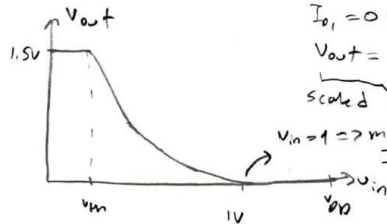
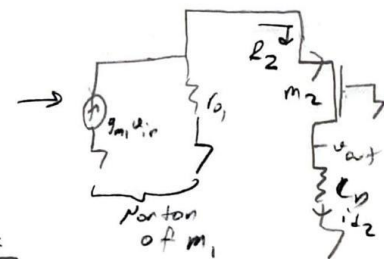
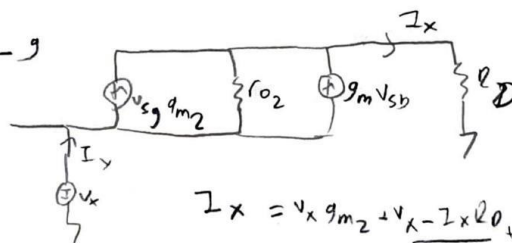
$$\frac{1}{2} = \frac{1}{2} \cdot 0.4 \cdot 10 \cdot (V_{in} - 0.5)^2 \Rightarrow V_{in} = 1 \text{ V}$$


 $I_{D1} = 0 \Rightarrow V_{out} = 0.5 \cdot 3 = 1.5 \text{ V}$ 
 $V_{out} = I_{D2} \cdot R_{D2}$ 

 scaled graph of  $I_{D2}$ 
 $V_{in} = 1 \Rightarrow \text{max current } (I_{D1})$   
 $I_{D2} = 0$  hence  $V_{out} = 0$ 


$$I_N = g_{m1} V_{in}$$

$$R_{th} = r_{o1}$$


 Find  $R_2 \rightarrow$ 


$$I_X = V_X g_{m2} + \frac{V_X - I_X R_D}{r_{o2}} + g_{m2} V_X = 0$$

$$R_2 = \frac{V_X}{I_X} = \left( 1 + \frac{R_D}{r_{o2}} \right) \cdot \left( g_{m2} + g_{m2} \frac{1}{r_{o2}} \right)^{-1} = \frac{r_{o2} + R_D}{1 + r_{o2} (g_{m2} + g_{m2})}$$

$$I_{D2} = g_{m1} V_{in} \cdot \frac{r_{o1}}{R_2 + r_{o1}}$$

$$V_{out} = I_{D2} \cdot R_D, A_v = \frac{g_{m1} r_{o1} R_D}{R_2 + r_{o1}}$$